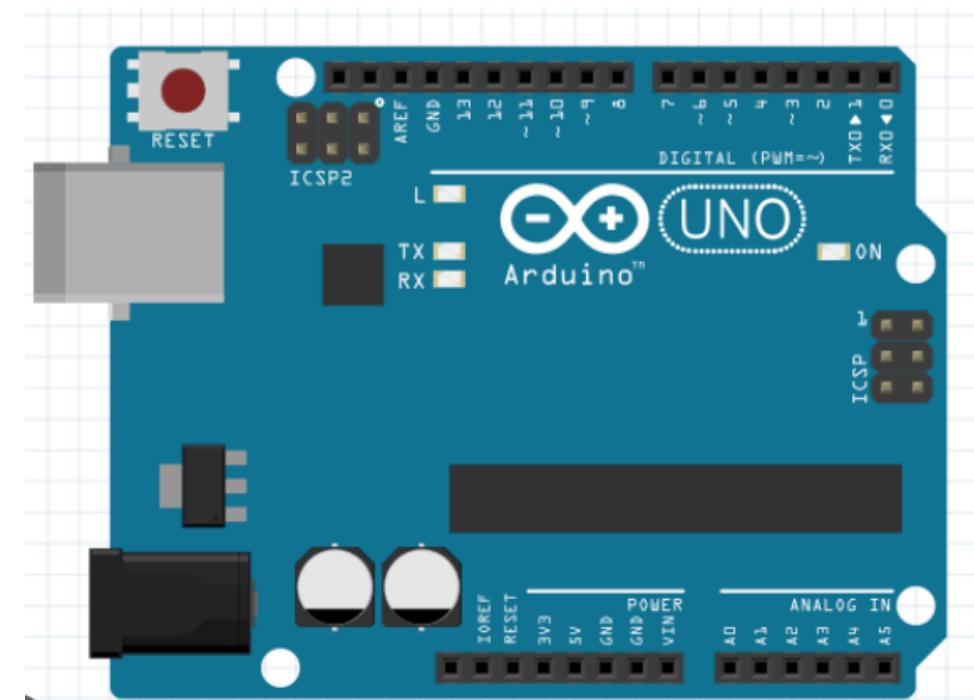



Arduino Uno R4 WiFi

x1




Arduino Uno R3

x1

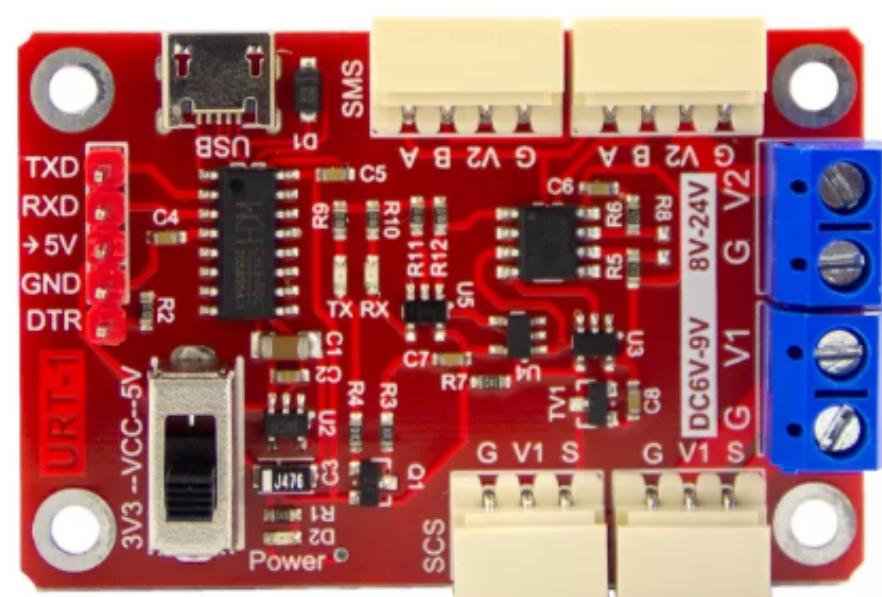

Feetech SCS SERVO CONTROLLER

x1

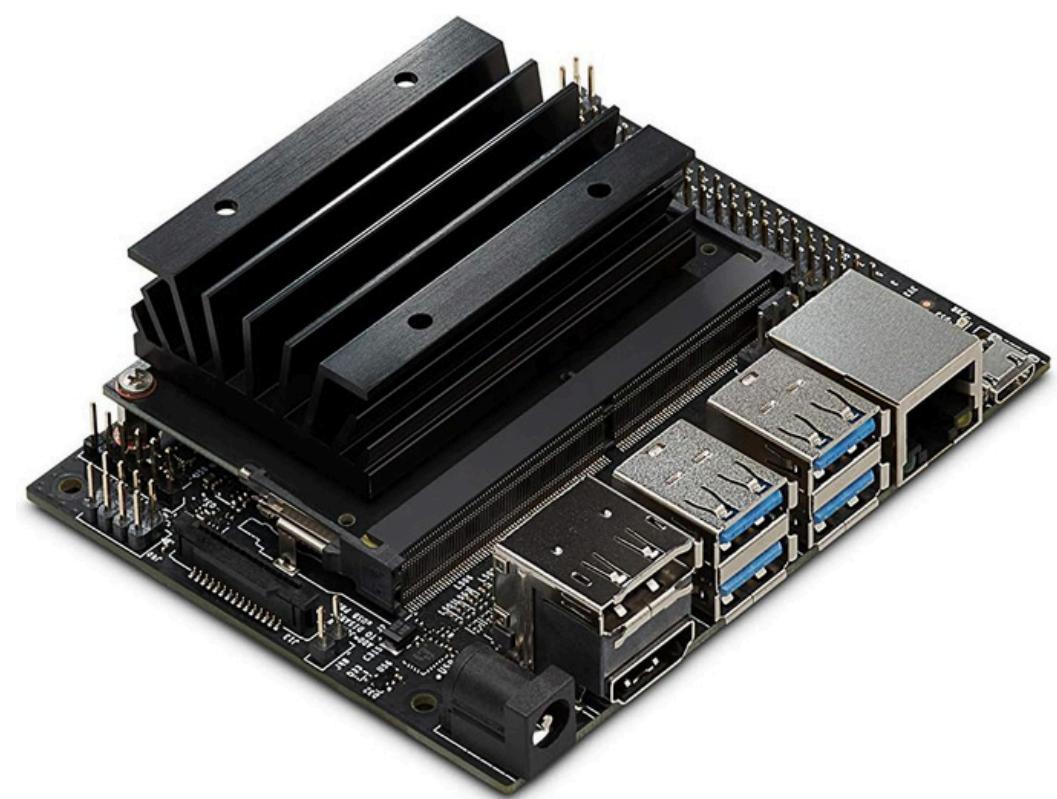


Jetson nano

x1



Servo scs15

x9

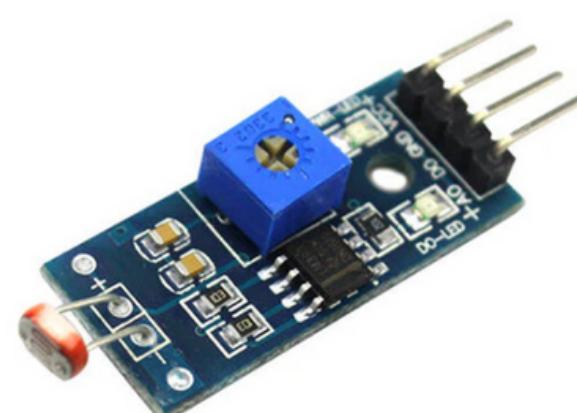

pixy2.1

x1


LDR Light Sensor Module

x1

Arduino R4 WiFi

connector


Feetech SCS SERVO CONTROLLER

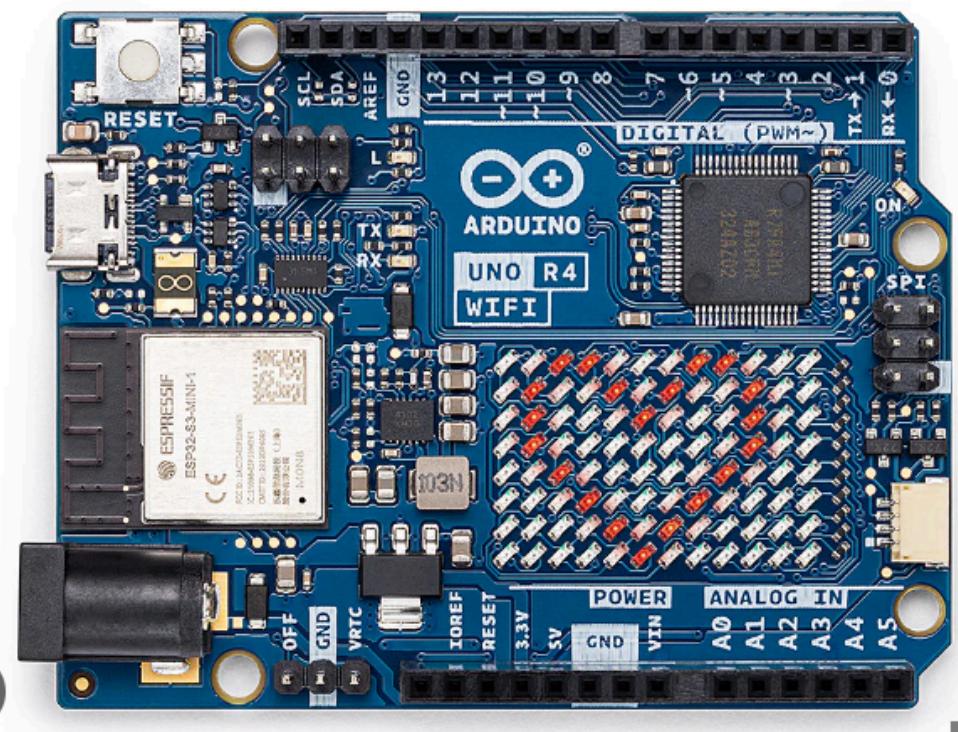

RX
TX
5V
GND

V
V
V
V

RX
TX
Vin
GND



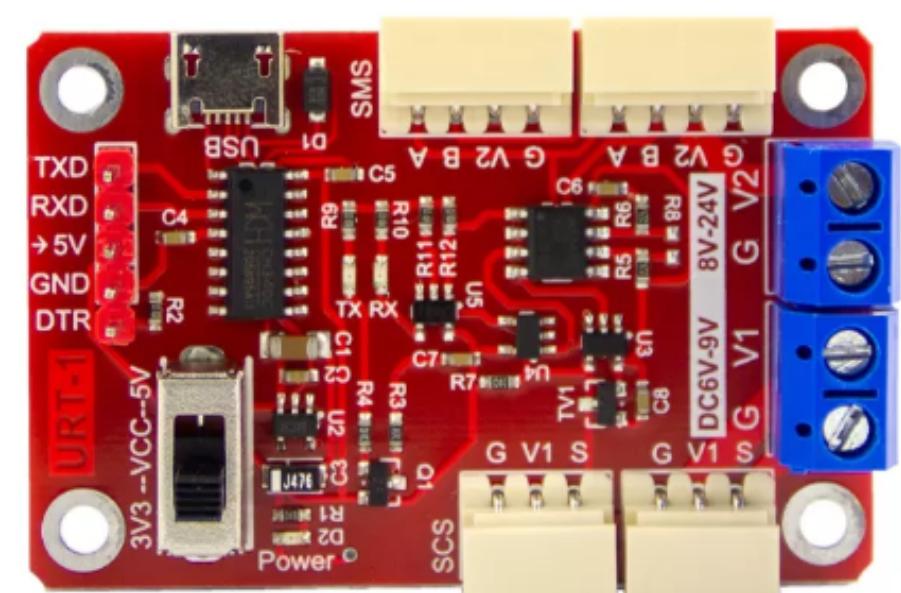


**V1 connect to
power supply 12v 6a
Gnd to Gnd**

Arduino Uno R3

connector


pixy2.1

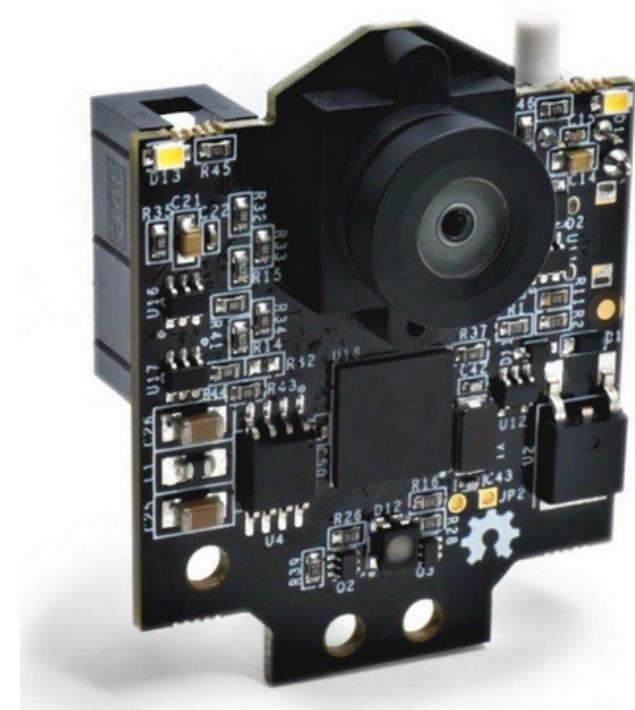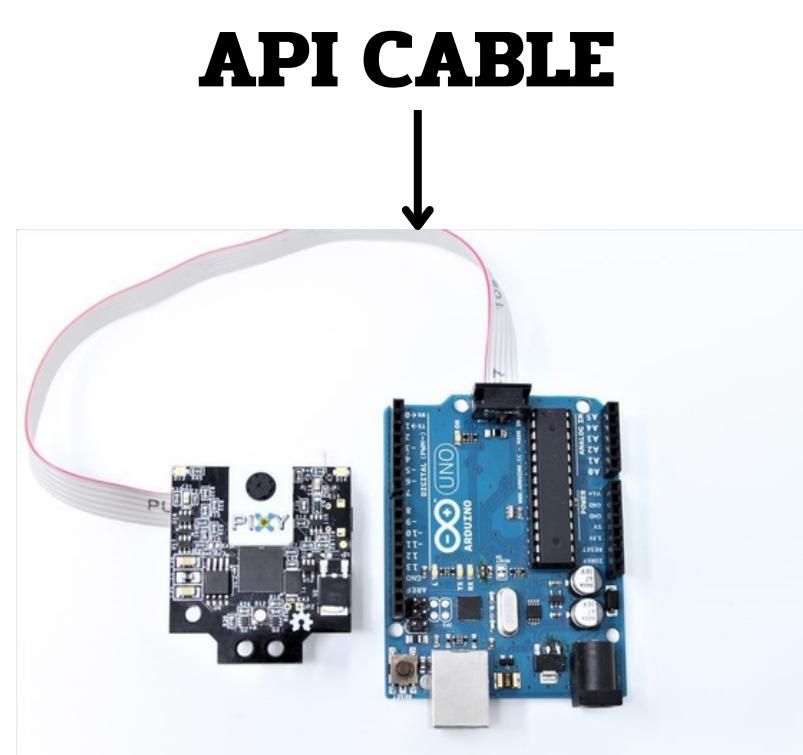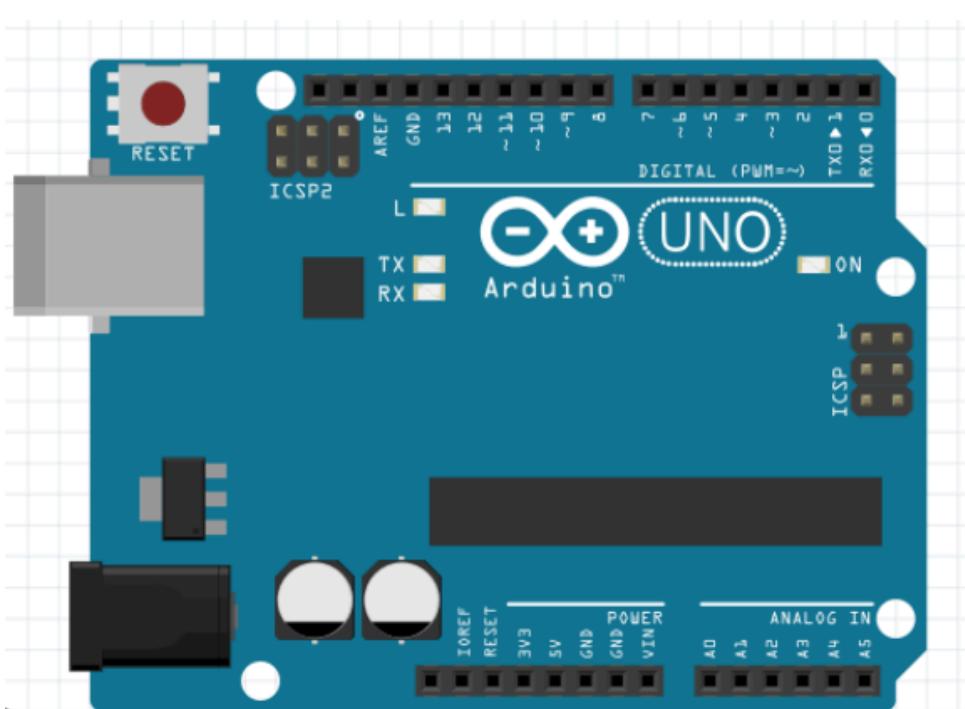

Feetech SCS SERVO CONTROLLER

connector


Servo scs15

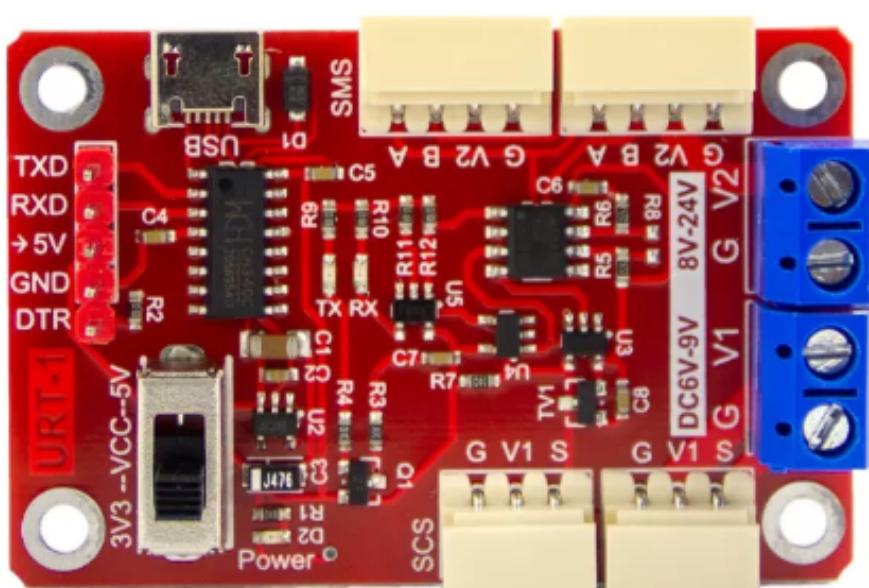

cable Keep connecting.



Arduino R4 WiFi

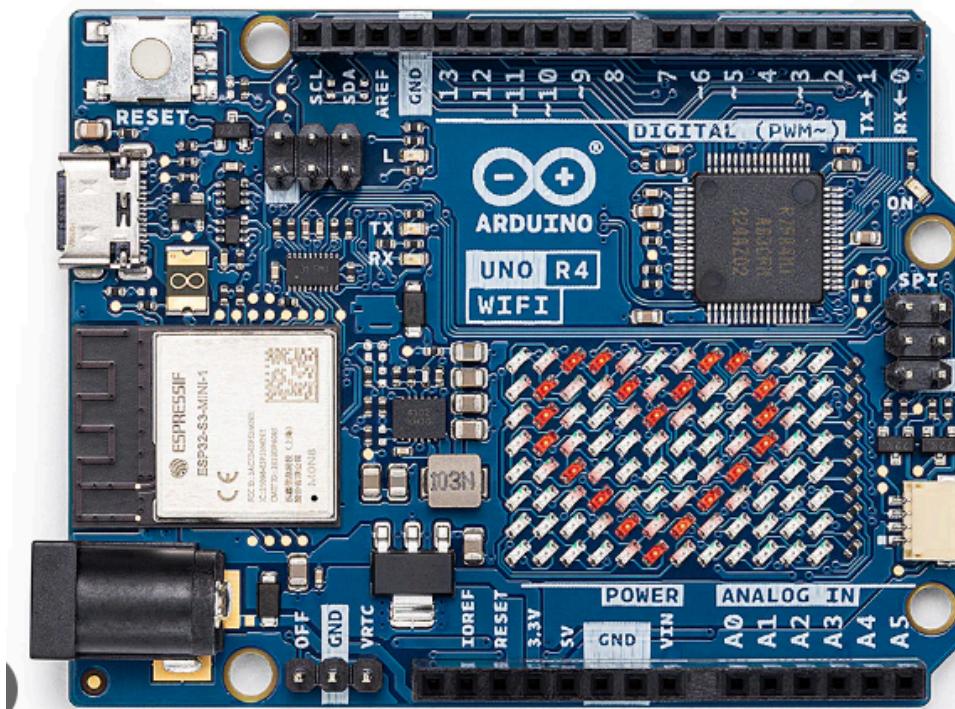




connector

LDR Light Sensor Module

**AO
3.3V
GND**


**V
V
V**

**AO
Vin
GND**

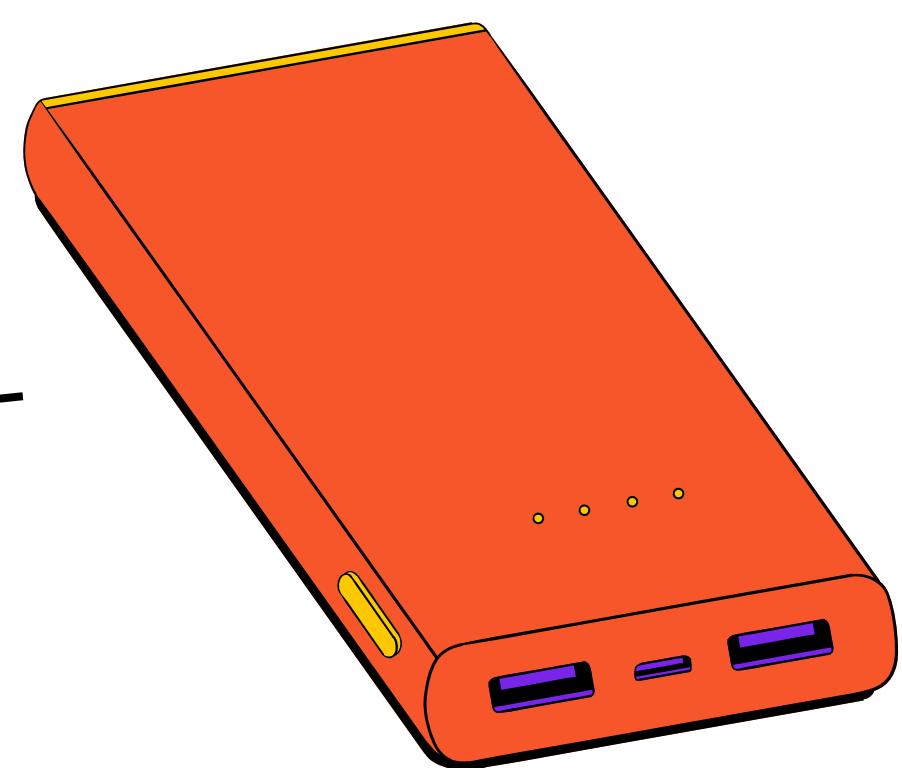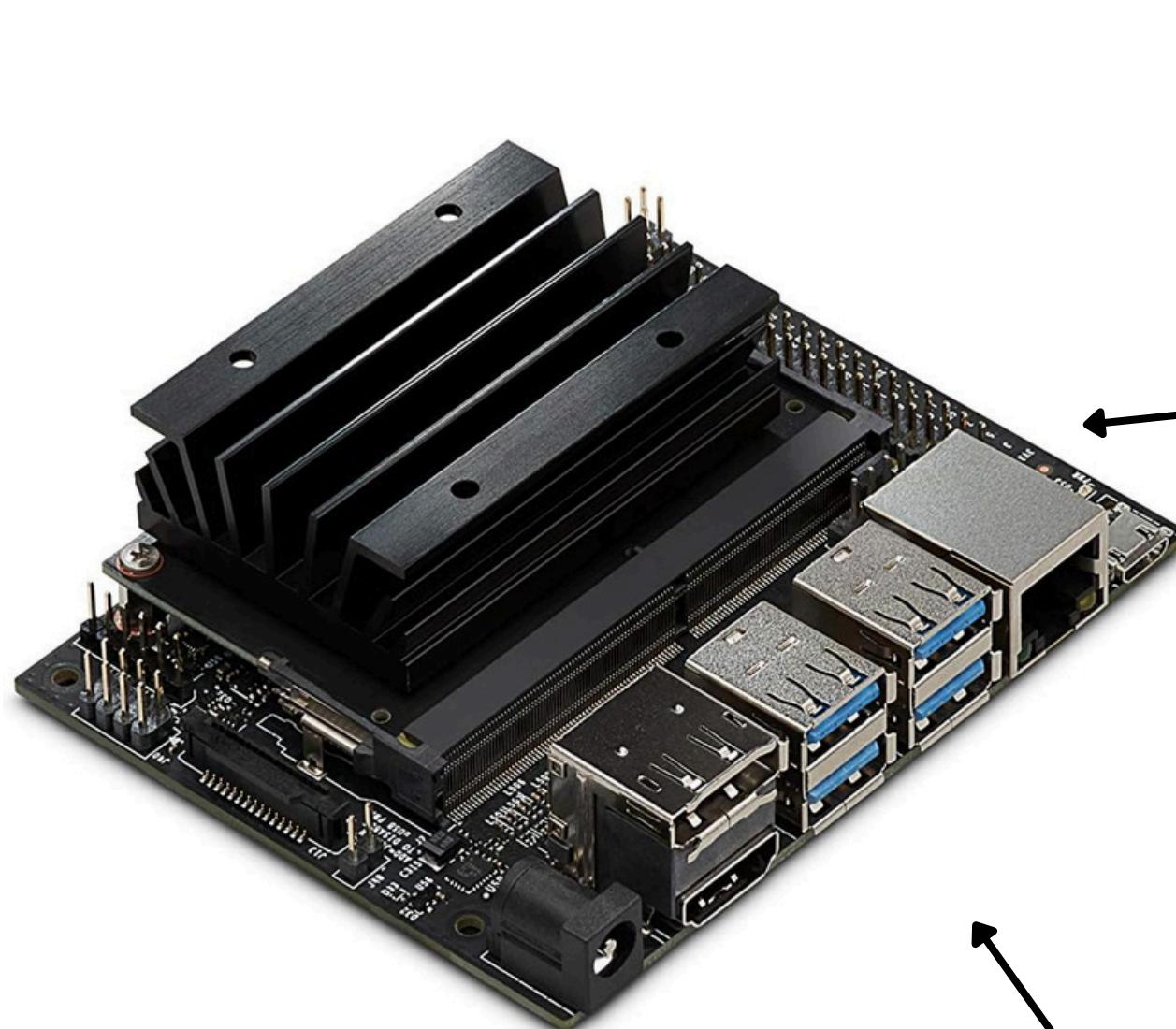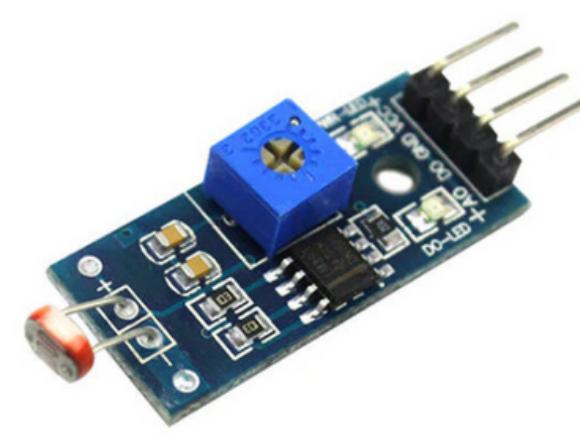

powerbank 5 V 2A

USB to USB 2.0

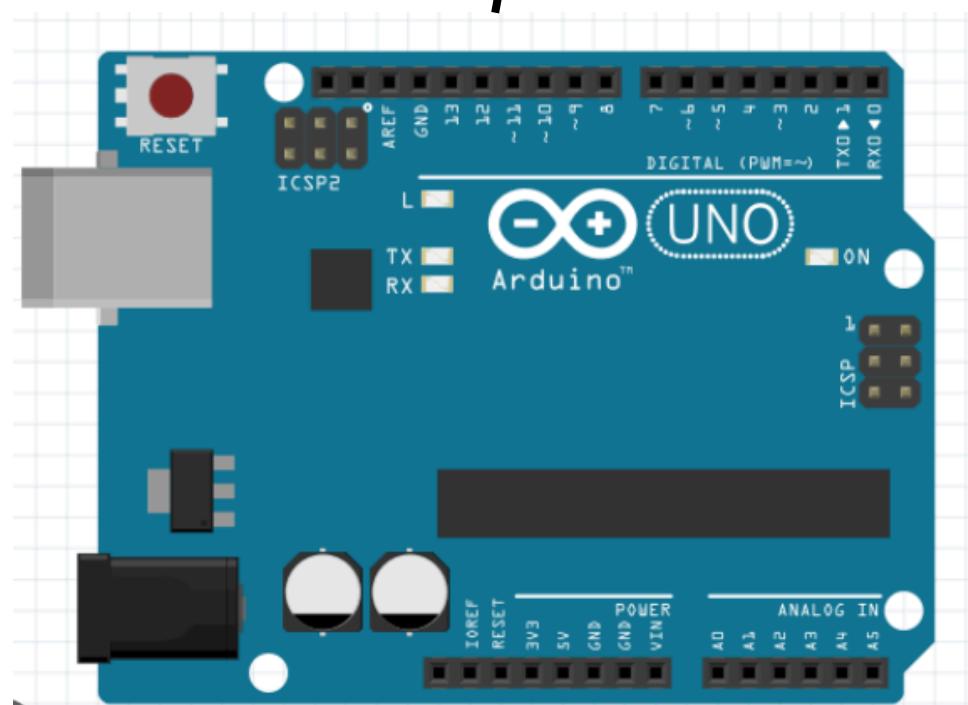

USB-C to USB 2.0

